



United International University

Name: Ibrahim Khalil

ID: 021 191 020

Subject: Electrical Wiring & Drafting

Section: A

Course Code: EEE 2200


Project

Project


PROJECT SPECIFICATION: 1600+ square ft 10 story building wiring

1. Civil Layout
2. Fitting & Fixture Layout
3. Conduit Layout
4. Light Loads Connection
5. Heavy Loads Connection
6. Switch Board Connection & SDB to MDB Connection
7. Antenna, Telephone Connection
8. Switchboard Calculation
9. Switchboard Connection & Groups
10. SDB & MDB Calculation
11. Breaker Selection for Groups
12. Distribution Board Diagram
13. Main Distribution Board Diagram
14. Calculation of SLD
15. SLD Design
16. Lightning Protection Setup
17. Earthing System
18. Light Calculation for Living Room
19. PV Calculation for 10 Story Building
20. PV System Calculation for 10 Story Building & Battery Sizing
21. Sizing of Solar Charge Controller & PV Inverter
22. Rooftop PV Design & Setup
23. Solar PV System-Model
24. Fire Safety System-Model

CIVIL LAYOUT

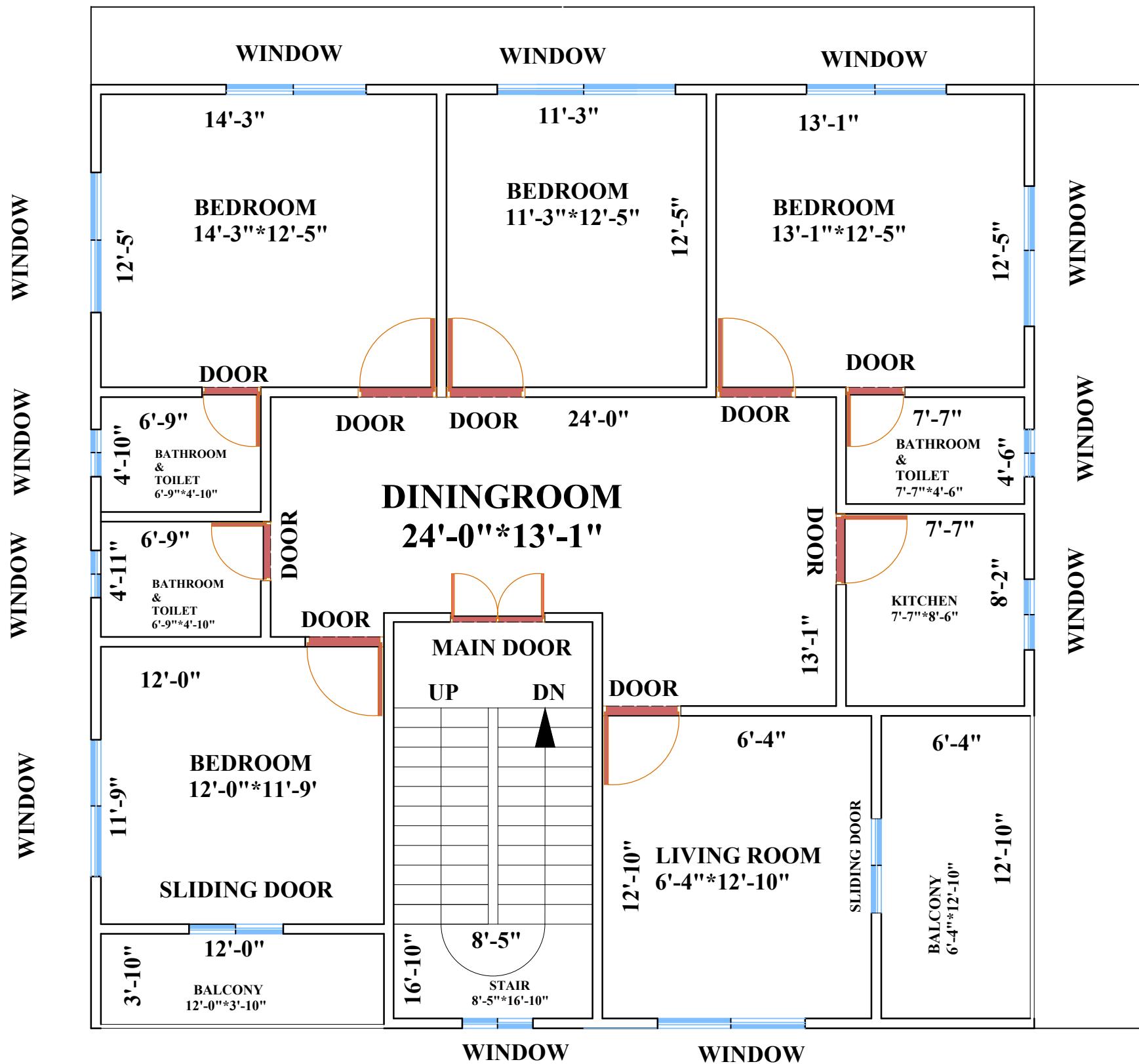


Fitting & Fixture Layout

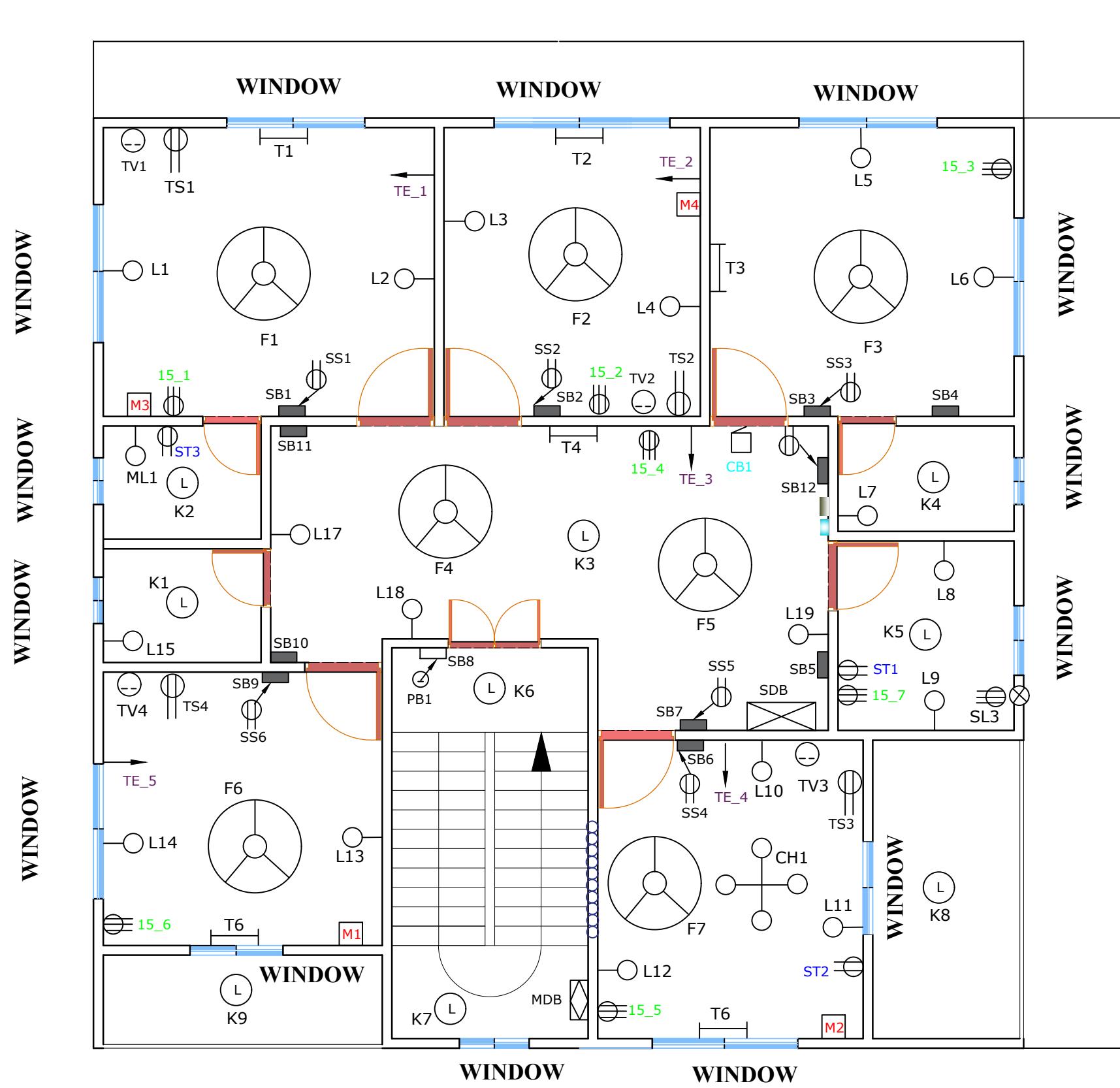


Symbol	Name
○—	Lintel level light
— —	Flurescent wall light
○	3 pin 15A socket at skirting level
○○	2 pin 5A socket at skirting level for TV
○○○	3 pin 5A socket at lintel level
○○	3 pin 5A socket at SB
○○○○	Celling Fan
□	Calling bell
(L)	K- Type light
⊗	Exhaust
(--)	2 pin TV antena Socket
(M)	AC
○○○○○	4 point Chandelier light
○○○○○○	Push button
→	Telephone Grommet
□□	Switch Board
□□□	SDB
□□□□	MDB
■■■■■■■■	Antena juncction box
■■■■■■■■	Telephone juncction box
○—	Mirror light

Conduit Layout

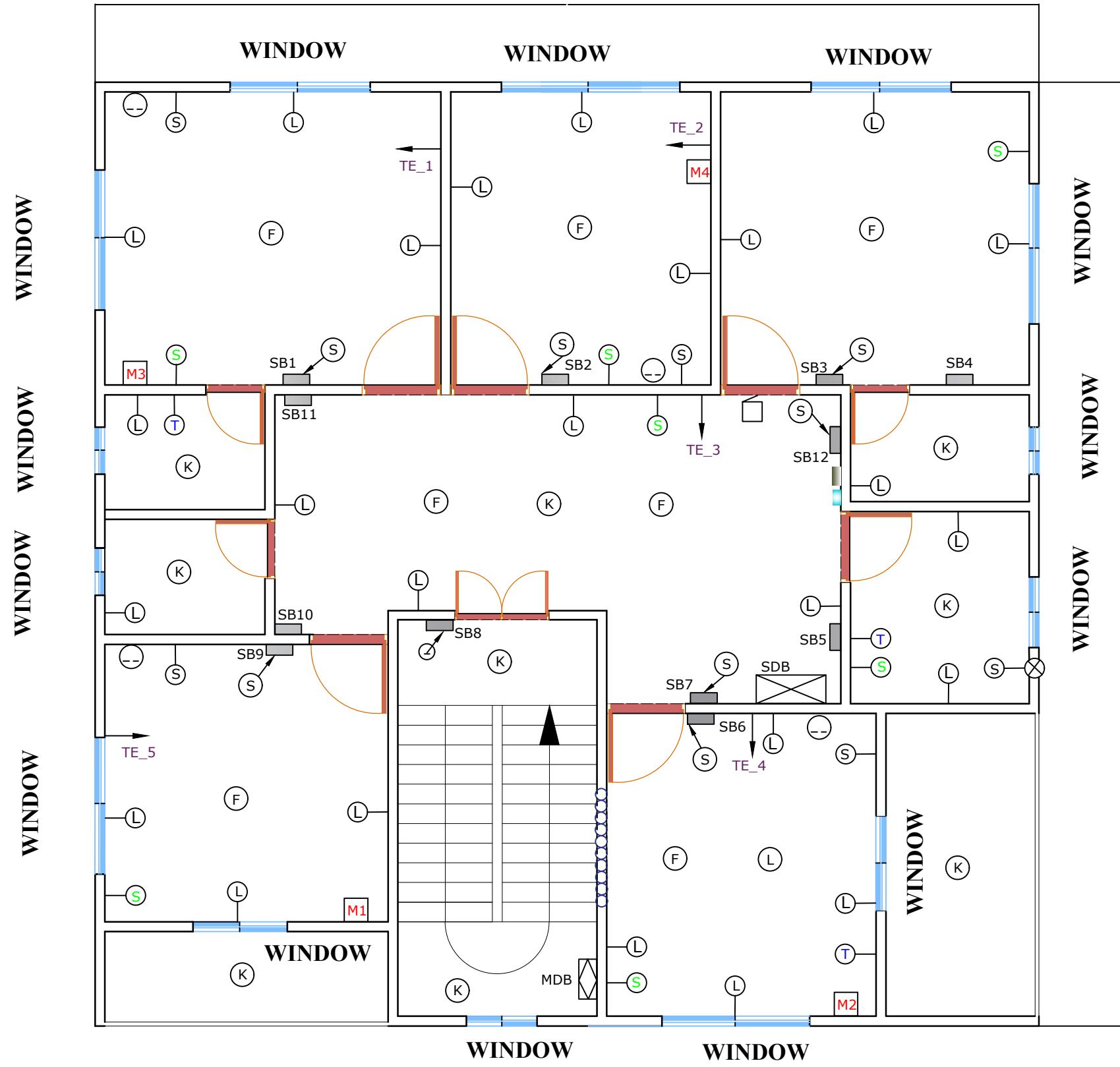

Symbol	Name
(L)	Lintel level light
(L)	Fluorescent wall light
(S)	3 pin 15A socket at skirting level
(S)	2 pin 5A socket at skirting level for TV
(S)	3 pin 5A socket at lintel level
(S)	3 pin 5A socket at SB
(F)	Celling Fan
(□)	Calling bell
(K)	K-Type light
(⊗)	Exhaust
(S)	2 pin TV antenna Socket
(M)	AC
(L)	4 point Chandelier light
(⊖)	Push button
→	Telephone Grommet
(□)	Switch Board
(SDB)	SDB
(MDB)	MDB
(■)	Antenna junction box
(■)	Telephone junction box
(L)	Mirror light

Light Load Connections

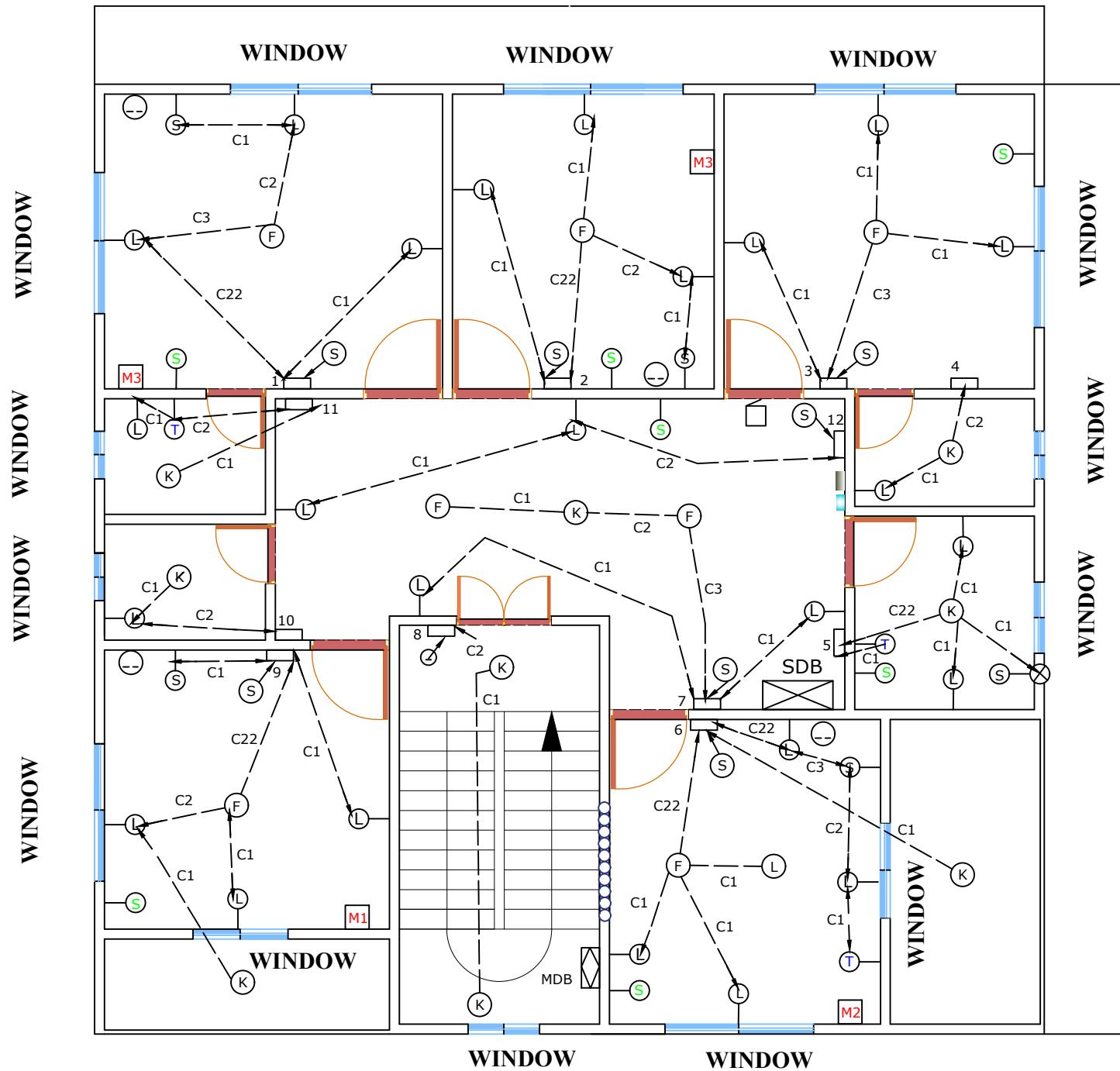


Wire Colour	Connection
Light Blue	Light Load

C1 - 2*1.5mm²
 C2 - 4*1.5mm²
 C22 - 2*(4*1.5mm²)
 C3 - 6*1.5mm²

Symbol	Name
(L)	Lintel level light
(L)	Flurescent wall light
(S)	3 pin 15A socket at skirting level
(S)	2 pin 5A socket at skirting level for TV
(S)	3 pin 5A socket at lintel level
(S)	3 pin 5A socket at SB
(F)	Celling Fan
(B)	Calling bell
(K)	K- Type light
(X)	Exhaust
(S)	2 pin TV antena Socket
(M)	AC
(L)	4 point Chandelier light
(P)	Push button
→	Telephone Grommet
□	Switch Board
◇	MDB
■	SDB
■■■■	Antena junciton box
■■■■■	Telephone junciton box
(L)	Mirror light

Heavy Load Connection

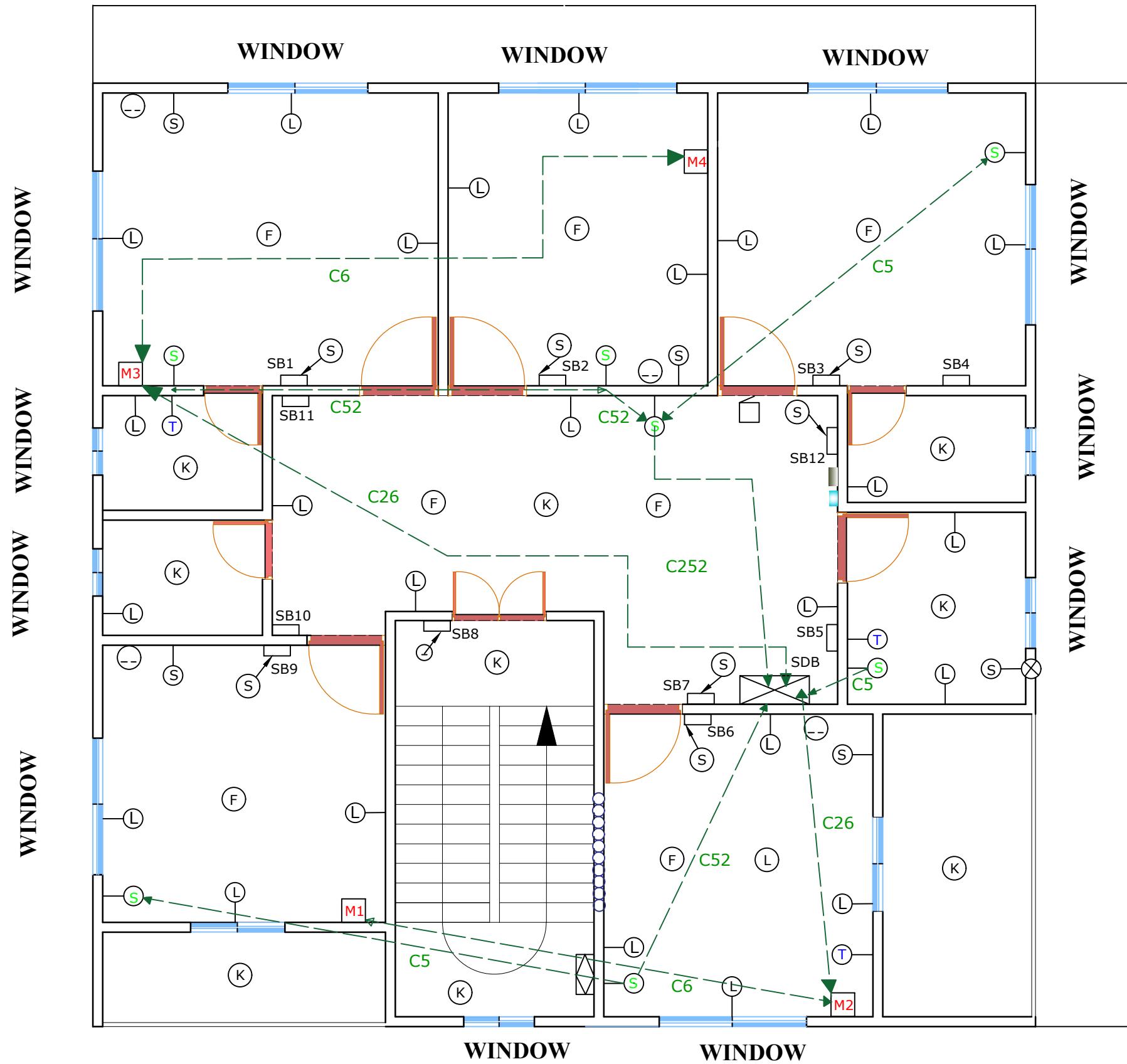


Wire colour	Connection
Dashed green	Heavy Load

Symbol	Name
(S)	3 pin 15A socket at skirting level
(M)	20A MSB at skirting level


Codes and descriptions:

- C5 - 2*4mm²,ECC (15A)
- C52 - 4*4mm²,ECC (15A)
- C252 -(6*4mm²,ECC)(15A)
- C6 - 2*6mm², ECC (20A)
- C26 - 4*6mm², ECC (20A)

Switch Board & SDB to MDB Connection

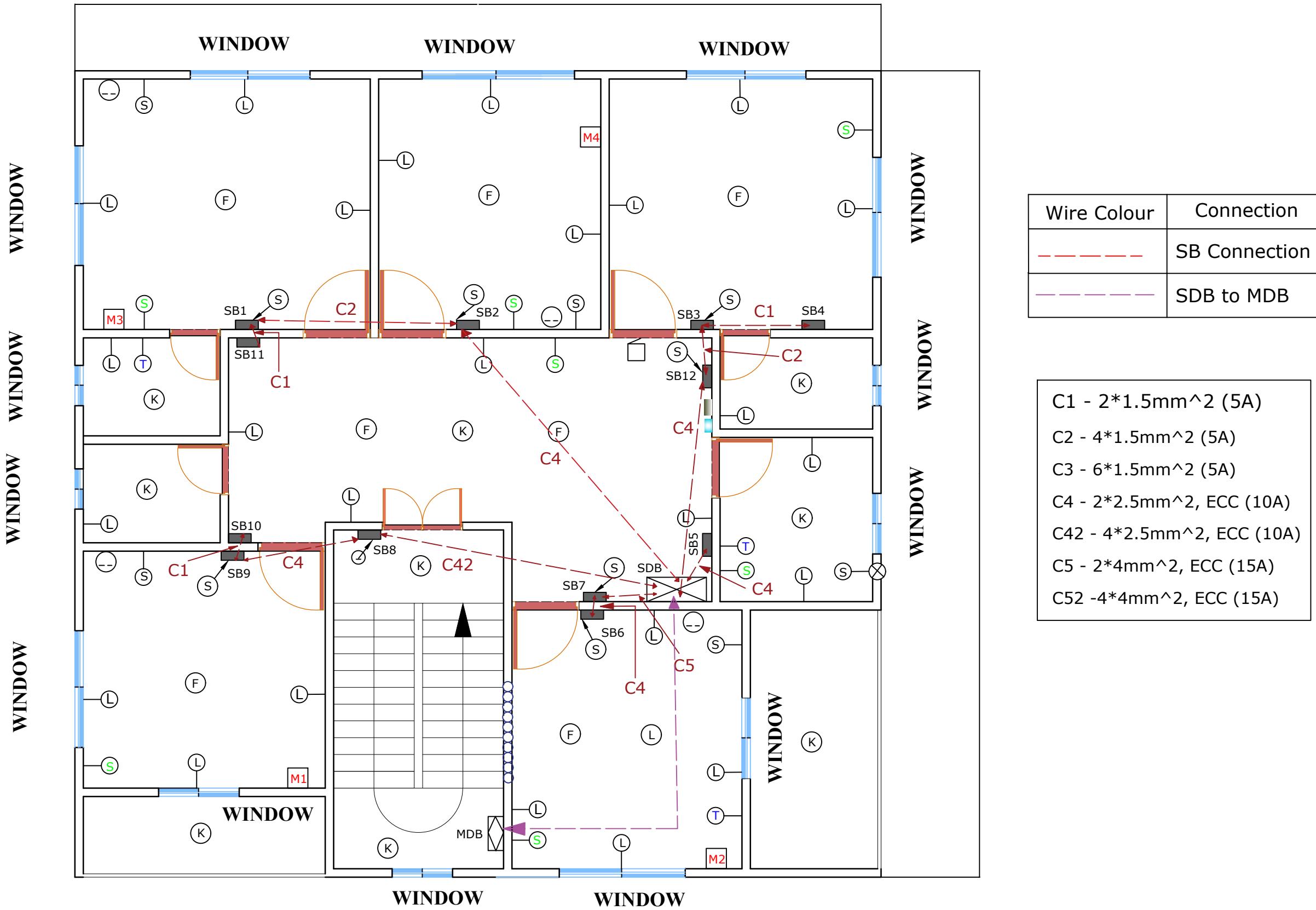

Antenna, Telephone Connection

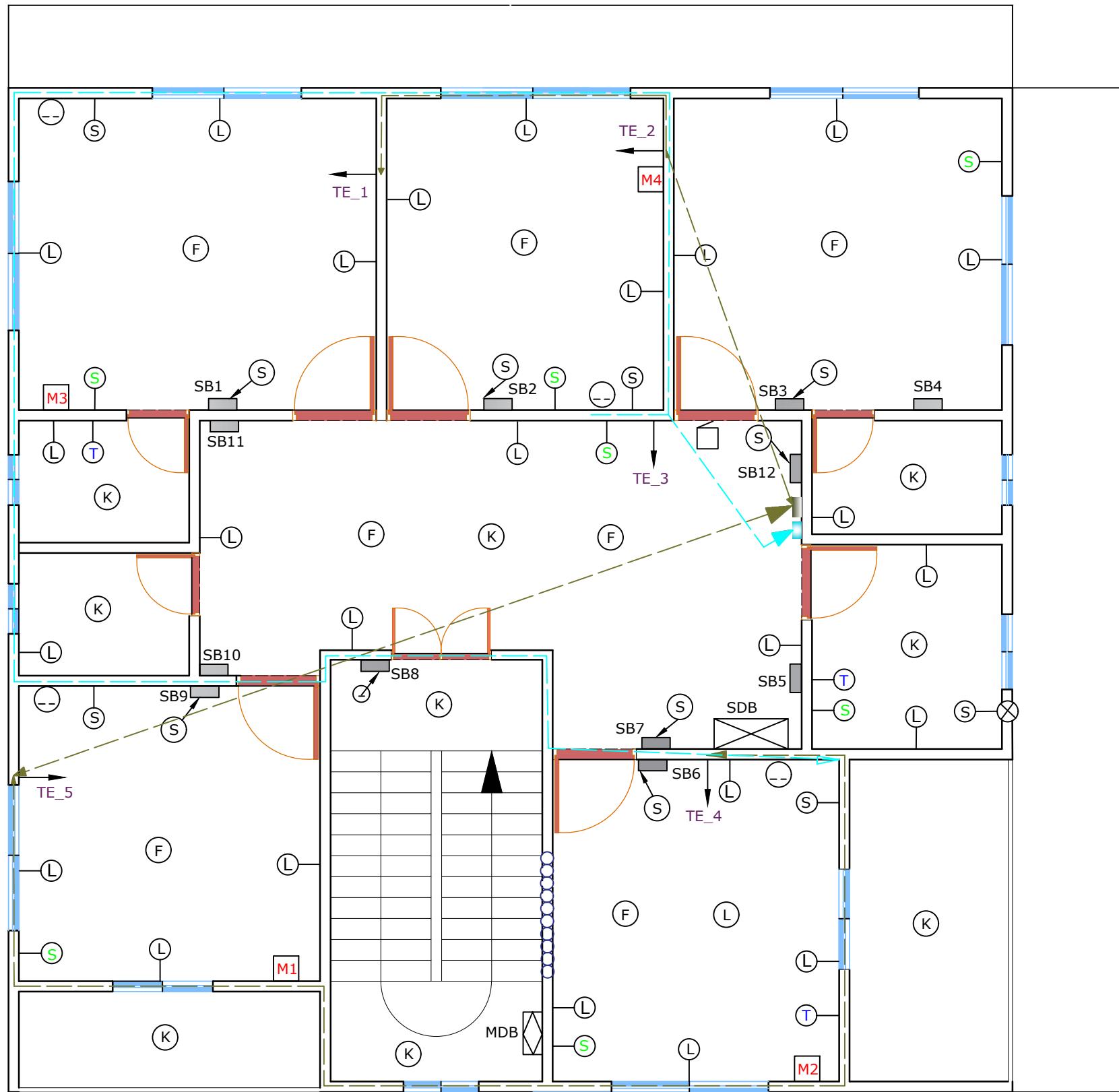

Symbol	Name
■	Antena junction box
■	Telephone junction box
×	SDB
◇	MDB
(-)	2 pin TV antena socket
→	Telephone grammet

Wire colour	Connection
Blue dashed	Antena junction line
Green dashed	Telephone line
Black dashed	SDB to MDB line

Switch Board Calculation

Switch Board-1

$$\begin{aligned} TS &= 500W \\ 2L &= 52 W \\ 1F &= 80W \\ 1T &= 40W \\ 1SS &= 500W \end{aligned}$$

$$\text{Total} = 1172W$$

$$\begin{aligned} P &= VICos(\theta) \\ \text{Here, } V &= 230V \\ \text{Let, P.F} &= 0.85 \\ I &= \frac{1172W}{230V*0.85} \\ &= 5.995A \end{aligned}$$

Switch Board-2

$$\begin{aligned} 1TS &= 500W \\ 2L &= 52 W \\ 1F &= 80W \\ 1T &= 40W \\ 1SS &= 500W \end{aligned}$$

$$\text{Total} = 1172W$$

$$\begin{aligned} P &= VICos(\theta) \\ \text{Here, } V &= 230V \\ \text{Let, P.F} &= 0.85 \\ I &= \frac{1172W}{230V*0.85} \\ &= 5.995A \end{aligned}$$

Switch Board-3

$$\begin{aligned} 2L &= 52 W \\ 1F &= 80W \\ 1T &= 40W \\ 1SS &= 500W \end{aligned}$$

$$\text{Total} = 672W$$

$$\begin{aligned} P &= VICos(\theta) \\ \text{Here, } V &= 230V \\ \text{Let, P.F} &= 0.85 \\ I &= \frac{672W}{240V*0.85} \\ &= 3.44A \end{aligned}$$

Switch Board-4

$$\begin{aligned} 1L &= 52 W \\ 1K &= 60W \end{aligned}$$

$$\text{Total} = 112W$$

$$\begin{aligned} P &= VICos(\theta) \\ \text{Here, } V &= 230V \\ \text{Let, P.F} &= 0.85 \\ I &= \frac{112W}{230*0.85V} \\ &= 0.57A \end{aligned}$$

Switch Board-5

$$\begin{aligned} 1ST &= 500W \\ 2L &= 52 W \\ 1K &= 60W \\ 1SL &= 500W \end{aligned}$$

$$\text{Total} = 1112W$$

$$\begin{aligned} P &= VICos(\theta) \\ \text{Here, } V &= 230V \\ \text{Let, P.F} &= 0.85 \\ I &= \frac{1112W}{230V*0.85} \\ &= 5.69A \end{aligned}$$

Switch Board-6

$$\begin{aligned} 1TS &= 500W \\ 3L &= 78 W \\ 1F &= 80W \\ 1T &= 40W \\ 1SS &= 500W \\ 1CH &= 80W \\ 1ST &= 500W \\ 1K &= 60W \end{aligned}$$

$$\text{Total} = 1838W$$

$$\begin{aligned} P &= VICos(\theta) \\ \text{Here, } V &= 230V \\ \text{Let, P.F} &= 0.85 \\ I &= \frac{1838W}{230V*0.85} \\ &= 9.4A \end{aligned}$$

Switch Board-7

$$\begin{aligned} 2L &= 52 W \\ 1K &= 60W \\ 2F &= 160W \\ 1SS &= 500W \end{aligned}$$

$$\text{Total} = 772W$$

$$\begin{aligned} P &= VICos(\theta) \\ \text{Here, } V &= 230V \\ \text{Let, P.F} &= 0.85 \\ I &= \frac{772W}{230V*0.85} \\ &= 4A \end{aligned}$$

Switch Board-8

$$\begin{aligned} 2K &= 120 W \\ 1PB &= 20W \end{aligned}$$

$$\text{Total} = 140W$$

$$\begin{aligned} P &= VICos(\theta) \\ \text{Here, } V &= 230V \\ \text{Let, P.F} &= 0.85 \\ I &= \frac{140W}{230V*0.85} \\ &= 0.72A \end{aligned}$$

Switch Board-9

$$\begin{aligned} TS &= 500W \\ 2L &= 52 W \\ 1F &= 80W \\ 1K &= 60W \\ 1T &= 40W \\ 1SS &= 500W \end{aligned}$$

$$\text{Total} = 1232W$$

$$\begin{aligned} P &= VICos(\theta) \\ \text{Here, } V &= 230V \\ \text{Let, P.F} &= 0.85 \\ I &= \frac{1232W}{230V*0.85} \\ &= 6.30A \end{aligned}$$

Switch Board-10

$$\begin{aligned} 1L &= 26W \\ 1K &= 60W \end{aligned}$$

$$\text{Total} = 86W$$

$$\begin{aligned} P &= VICos(\theta) \\ \text{Here, } V &= 230V \\ \text{Let, P.F} &= 0.85 \\ I &= \frac{86W}{230V*0.85} \\ &= 0.44A \end{aligned}$$

Switch Board-11

$$\begin{aligned} 1ST &= 500W \\ 1L &= 26 W \\ 1K &= 60W \end{aligned}$$

$$\text{Total} = 586W$$

$$\begin{aligned} P &= VICos(\theta) \\ \text{Here, } V &= 230V \\ \text{Let, P.F} &= 0.85 \\ I &= \frac{586W}{230V*0.85} \\ &= 3A \end{aligned}$$


Switch Board-12

$$\begin{aligned} 1L &= 26W \\ 1T &= 40W \\ 1SS &= 500W \end{aligned}$$

$$\text{Total} = 566W$$

$$\begin{aligned} P &= VICos(\theta) \\ \text{Here, } V &= 230V \\ \text{Let, P.F} &= 0.85 \\ I &= \frac{566W}{230V*0.85} \\ &= 2.8951A \end{aligned}$$

Switch Board Connection Diagram & Groups

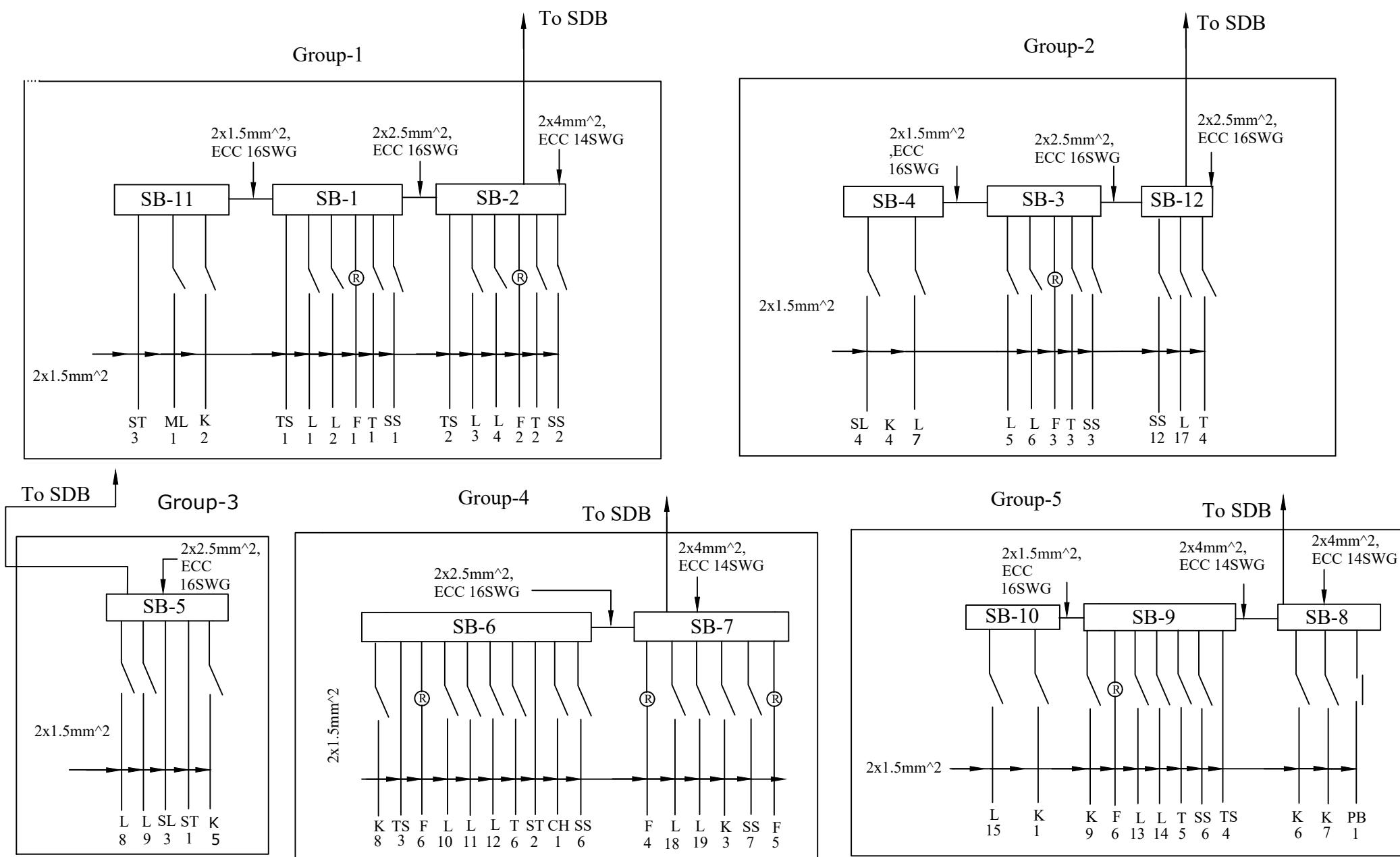

Calculation for SDB

Light Loads

PLL

$$\begin{aligned} &= (1172+1172+672+112+1112+1838+772+140+1232+86 \\ &\quad + 586+566) \text{ W} \\ &= 9374 \text{ W} \end{aligned}$$

Heavy Loads

PHL-15A

$$7*15 \text{ S} = 7*1000 \text{ W} \quad [\text{Assuming } 1000] \\ = 7000 \text{ W}$$

PHL-20A

$$\begin{aligned} 4 * M &= 4 * 2.25 \text{ KW} \\ &= 9 \text{ KW} \\ &= 9000 \text{ W} \end{aligned}$$

$$\begin{aligned} P_{\text{total}} &= PLL * 0.6 + PHL_15A * 0.7 + PHL_20 * 1 \\ &= 9374 * 0.6 + 7000 * 0.7 + 9000 * 1 \\ &= 19524.4 \text{ W} \\ &= 19.5244 \text{ KW} \end{aligned}$$

48 KW > 19.5244 KW > 9 KW, [So need 3 phase 415V line to line]

$$\begin{aligned} P3q &= 1.7320 * VL * IL * \cos(\theta) \\ \Rightarrow IL &= \frac{P3q}{1.7320 * VL * 0.85} \end{aligned}$$

$$\begin{aligned} &= \frac{19524.4 \text{ W}}{1.7320 * 415 * 0.85} \\ &= 31.9567 \text{ A} \end{aligned}$$

$$\begin{aligned} \text{With Spare, } I &= 31.9567 \text{ A} + 10 \text{ A} \\ &= 41.9567 \text{ A} \end{aligned}$$

With safety factor,

$$\begin{aligned} ICB &= I * S.F \\ &= 50.61 \text{ A} * 1.25 \\ &= 52.44 \text{ A} \end{aligned}$$

Now, I choose 60A TP Circuit Breaker

Calculation for MDB

Each Unit = 19.5244 KW

$$\begin{aligned} \text{For, 10 Units} &= 10 * 19.5244 \text{ KW} \\ &= 195.244 \text{ KW} \end{aligned}$$

I choose 1 Water Pump.

So,

$$\begin{aligned} 1 \text{ Water Pump} &= 3 * 746 \text{ W} \quad [1 \text{ HP} = 746 \text{ W}] \\ &= 2238 \text{ W} \\ &= 2.238 \text{ KW} \end{aligned}$$

For Lift,

I choose 900KG Lift

Speed = 1.8m/s

Motor Capacity, P = 9.7 KW

MCCB Capacity = 30A

$$\begin{aligned} P_{\text{total}} &= 195.244 \text{ KW} + 2.238 \text{ KW} + 9.7 \text{ KW} \\ &= 207.182 \text{ KW} \end{aligned}$$

$$\begin{aligned} IL &= \frac{207.182 * 1000}{1.7520 * 415 * 0.98} \quad \left| \begin{array}{l} \text{Let,} \\ \cos(\theta) = 0.98 \end{array} \right. \\ &= 290.766 \text{ A} \end{aligned}$$

I choose 300 A TP MCCB

Breaker Selection for Groups

Group-1

SB- 1, SB- 2, SB- 11

$$= 5.995A + 5.995A + 3A$$

$$= 14.99A$$

So, I choose 15A breaker

Group-2

SB- 3, SB- 4, SB- 12

$$= 3.44A + 0.57A + 2.895A$$

$$= 6.9A$$

So, I choose 10A breaker

Group-3

SB- 5

$$= 5.67A$$

So, I choose 10A breaker

Group-4

SB- 6, SB- 7

$$= 9.4A + 2.88A$$

$$= 13.4A$$

So, I choose 15A breaker


Group-5

SB- 8, SB- 9, SB- 10


$$= 0.72A + 6.30A + 0.44A$$

$$= 7.46A$$

So, I choose 10A breaker

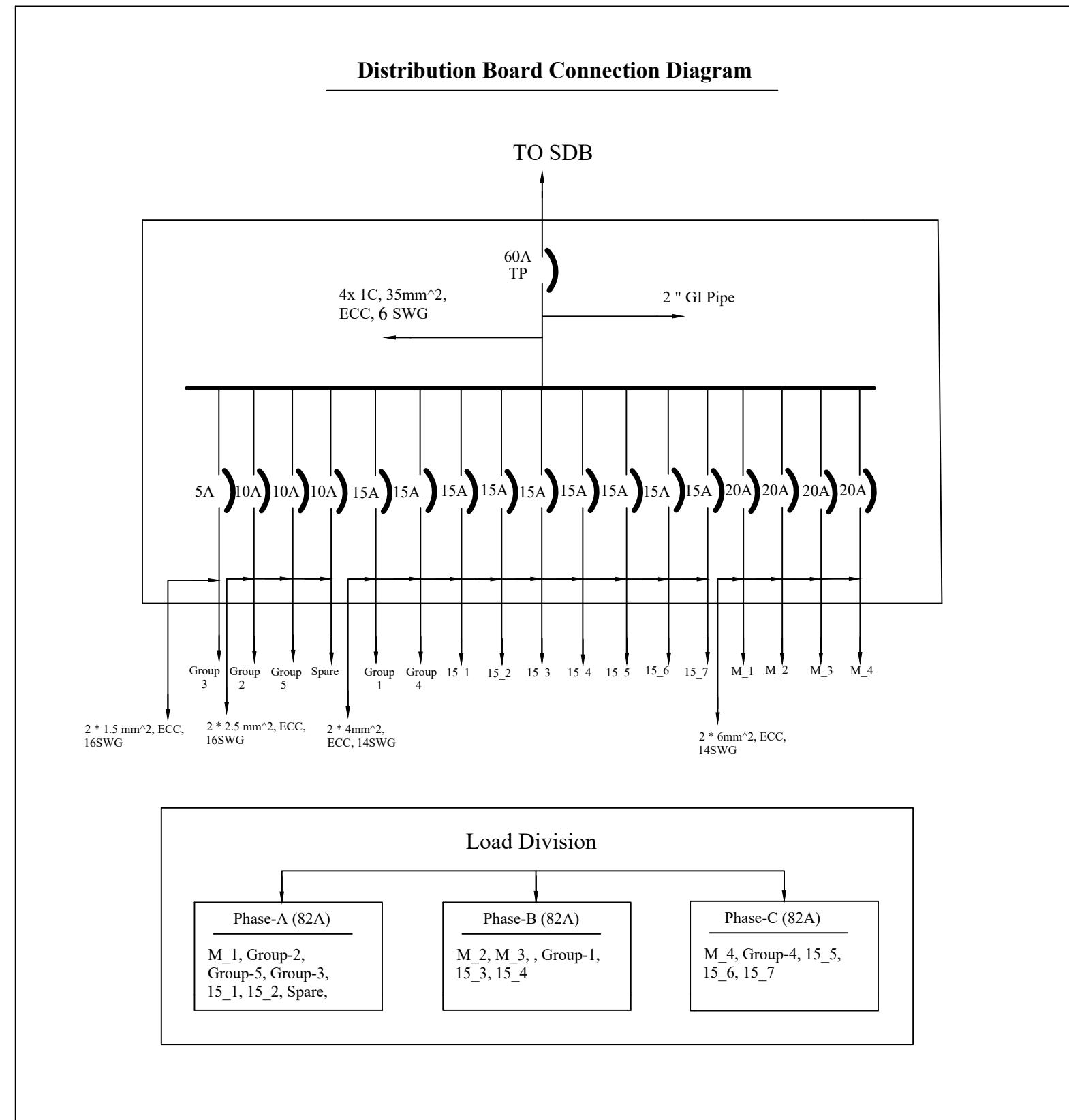

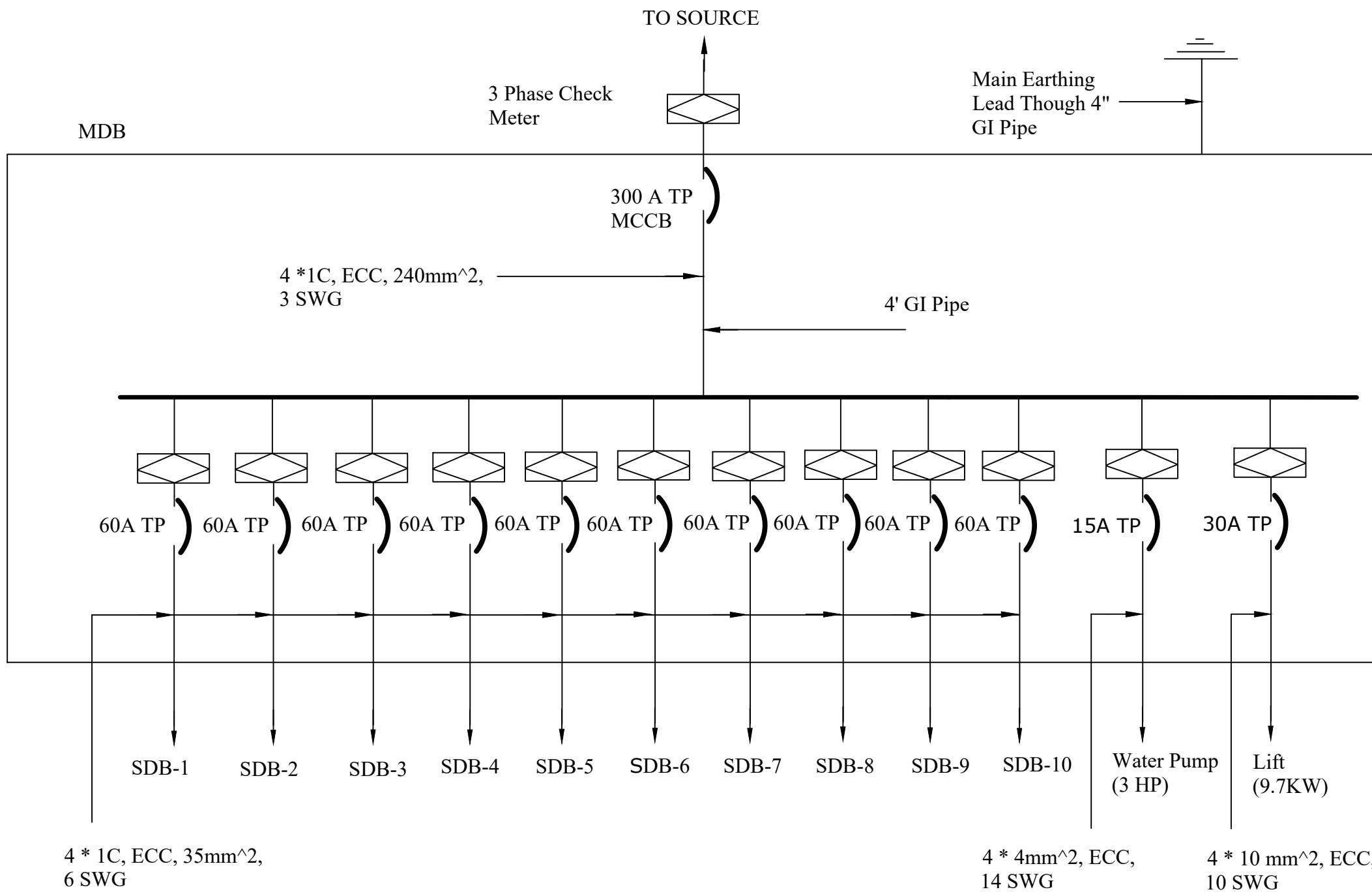Main Distribution Board Connection Diagram



Calculation of SLD

MDB Total Power, Ptotal = 207.182 KW

Transformer,

$$= \frac{P_{\text{total}} * 80\% * \text{S.F.}}{\text{P.F.}}$$

P.F. = 0.98


$$= \frac{207.182 * 0.8 * 1.25}{0.98}$$

S.F. = 1.25



$$= 211.41 \text{ KVA}$$

I am choosing 215 KVA transformer


11 KV Line

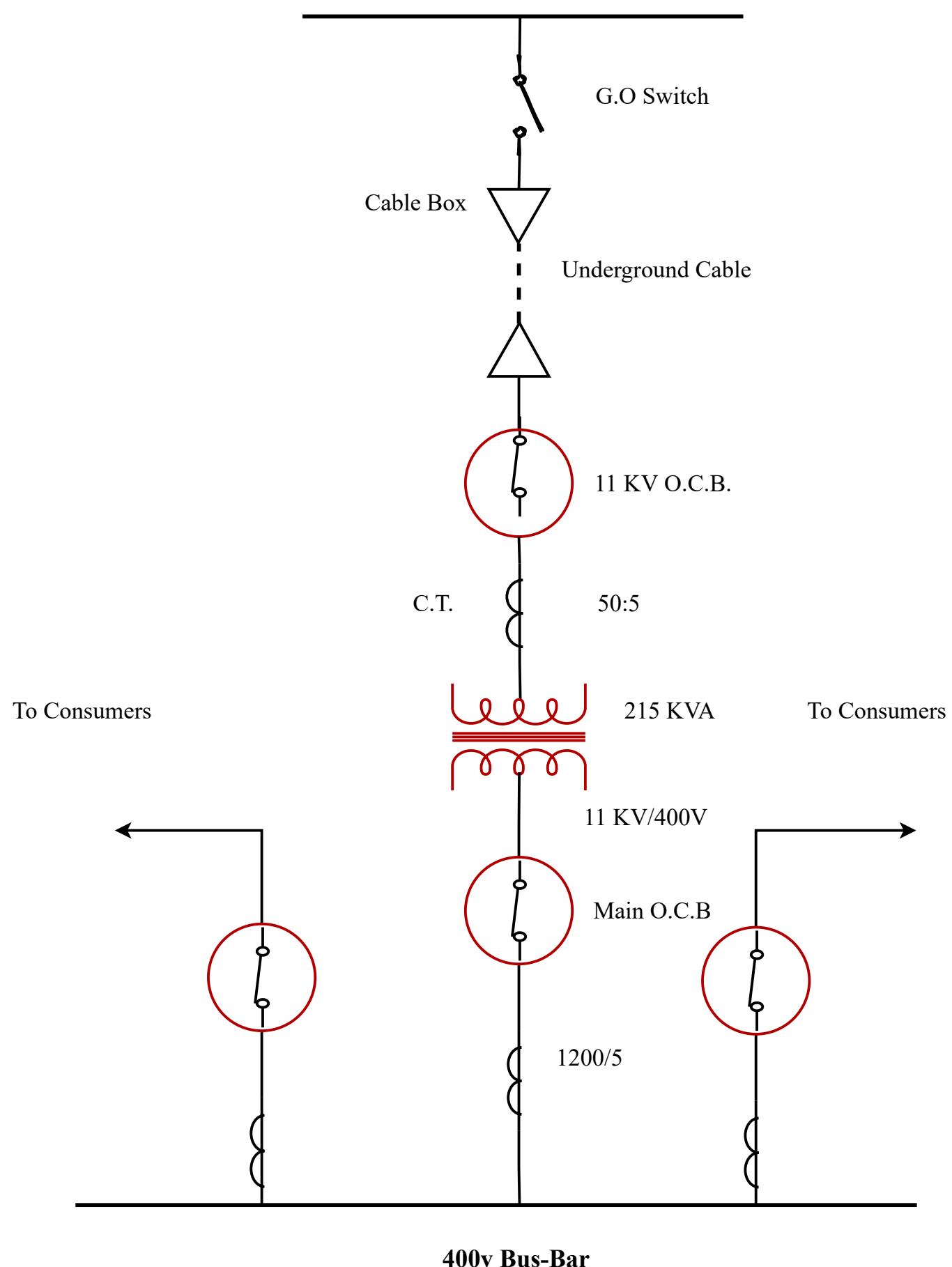

Lighting Protection Setup

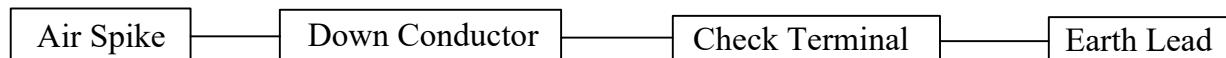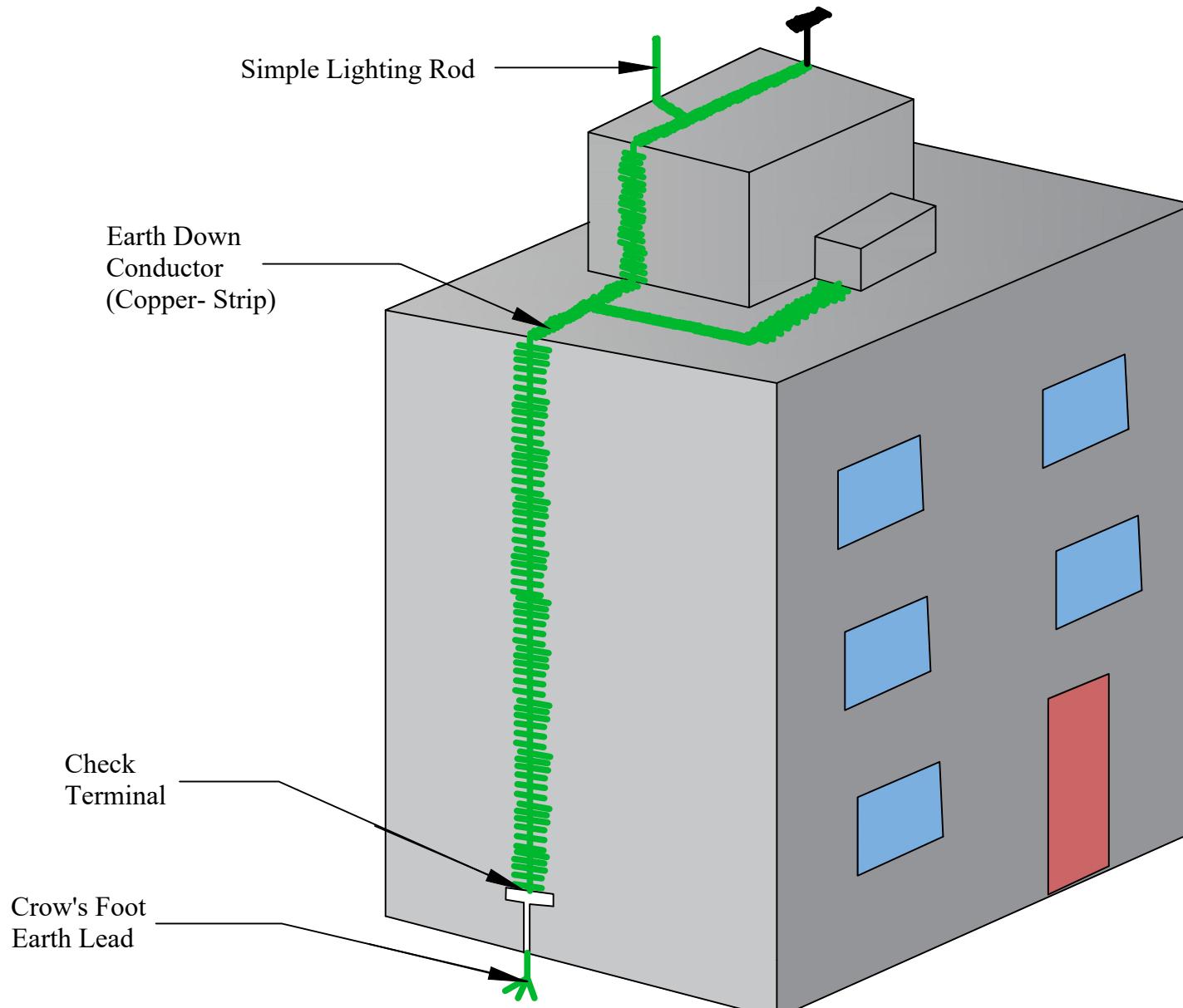

Earthing System

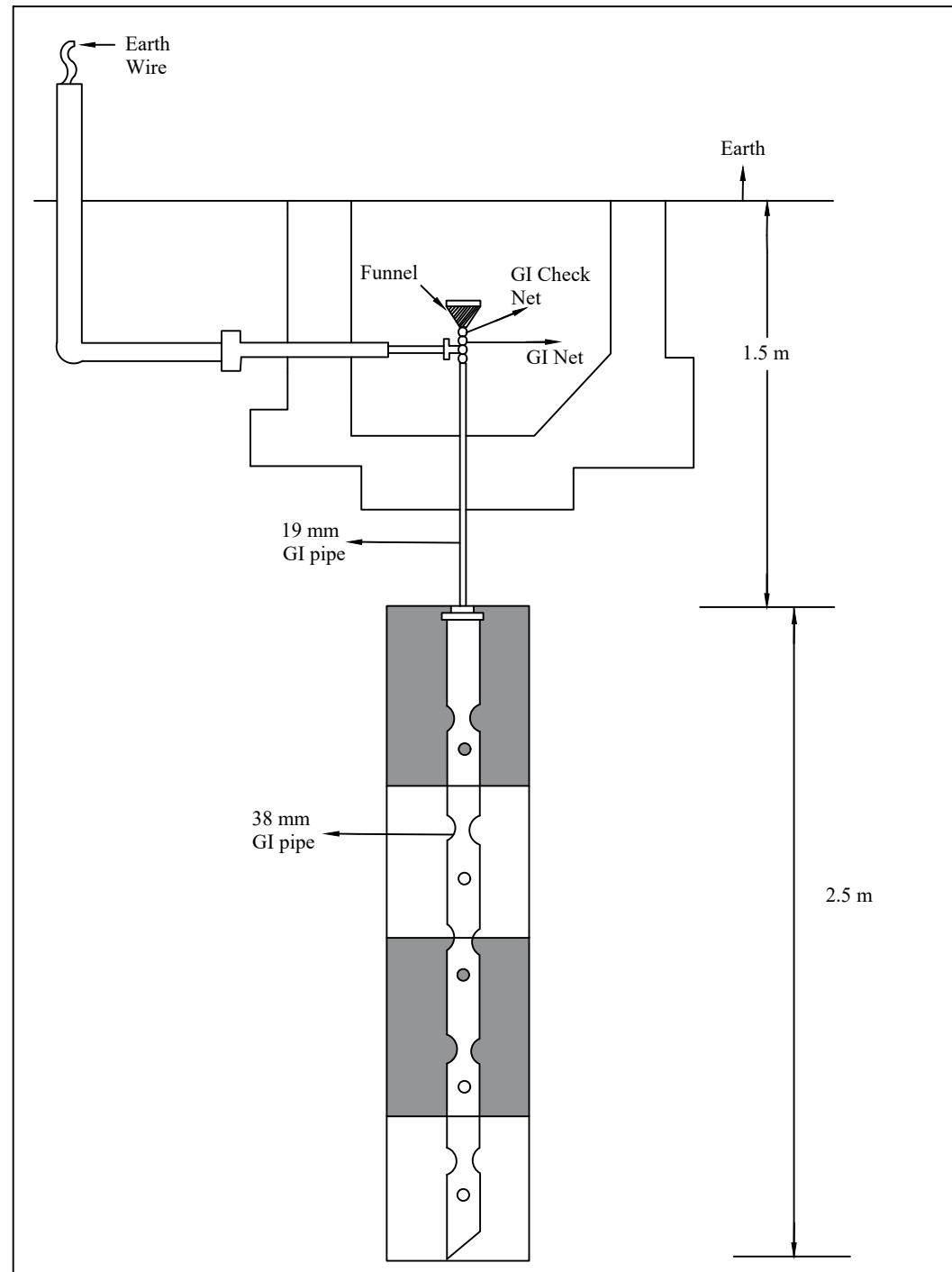

I choose Pipe Earthing System for this design.
For this type earthing,
-Need GI pipe
-Need permanent wet soil
-Need coal and salt

Earth Continuity Conductor (ECC)

Connecting Point

Earthing Lead

Earth Electrode

Earth electrode and earthing lead are same material

The current rating for this building is 290.766 A

So, ECC size is 3 SWG &
Main Earthing lead size is 3 SWG

Main Earthing lead though 3.5" G.I
pipe

By using 3 point method,
we find that the earth resistance
is 1 ohm

Light Calculation for Living Room

$$\begin{aligned} L &= 6.4 \text{ feet} \\ &= 6.4/3.281 \\ &= 1.96 \text{ m} \end{aligned}$$

$$\begin{aligned} W &= 12.10 \text{ feet} \\ &= 12.10/3.281 \\ &= 3.7 \text{ m} \end{aligned}$$

Let,

For living room, $E = 70$ lux

I am choosing LED lamp
Lamp $P = 11W$
Lumen = 806 lm

Now,
Room Height = 3.30 m
Working height = 0.5 m
 $H = 3.30 - 0.5$
= 2.80m

Room index,

$$\begin{aligned} RI &= \frac{L * W}{H * (L + W)} \\ &= \frac{1.96 * 3.7}{2.80 * (1.96 + 3.7)} \\ &= 0.46 \\ &\approx 0.75 \end{aligned}$$

Room Reflectances,
70-50-20
So,

$UF = 0.36$
Let, $LLF = 0.8$


Number of lights,

$$\begin{aligned} N &= \frac{E * A}{F * UF * LLF} \\ &= \frac{70 * (1.96 * 3.7)}{806 * 0.36 * 0.8} \\ &= 2.2 \\ &\approx 3 \end{aligned}$$

Distance,

$$\begin{aligned} D &= \frac{L}{L_H + 1} \\ &= \frac{1.96}{1+1} \\ &= 0.98 \text{ m} \end{aligned}$$

$L_H = 1$ light
 $L_V = 1$ light

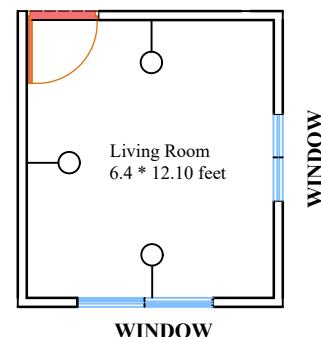

PV System Calculation For 10 Story Building

Room	CFL Lamp	K-Type	FL Lamp	Fan	Tv	ML
Dinning	3	1	1	2	0	0
Living	3	0	1	1	1	0
Toilet/Bath	2	3	0	0	0	1
Bed Room	8	0	4	4	3	0
Corridor	0	2	0	0	0	0
Kitchen	2	1	0	0	0	0
Balcony	0	2	0	0	0	0
Total	18	9	6	7	4	1

Name	Number	Watt	Hour	Energy
CFL Lamp	18	26	10	4680
K-Type	9	60	6	3240
FL lamp	6	40	9	2160
Fan	7	80	9	5040
TV	4	200	4	3200
ML	1	20	2	40
Total		18360 W		

For 10 units (5% load),

$$P = 18360 * 10 * 0.05$$

$$= 9180 \text{ W}$$

Total power consumption per floor,

$$= 18*26 + 9*60 + 6*40 + 7*80 + 4*200 + 1*20$$

$$= 2628 \text{ W}$$

Total power consumption for entire building with 5% load,

$$= 2628 * 10 * 0.05$$

$$= 1314 \text{ W}$$

$$= 1.314 \text{ KW}$$

Here, $1.314 < 1.5 \text{ KW}$,
So, System Nominal Voltage is 12V

PV System Calculation For 10 Story Building Battery Sizing

I am choosing,

Suncare 250W-12V Solar Panel

$P_{max} = 250 \text{ W}$
 Nominal Voltage = 12 V
 $ISC = 8.95 \text{ A}$
 Maximum Current = 8.957 A
 $V_{oc} = 37.25 \text{ V}$
 Maximum voltage = 29.94 V

Parallel Modules,

$$\begin{aligned}
 &= \frac{\text{Total Energy in WH}}{T_{peak \text{ Solar}} * n_{PV} * n_{Inv} * n_{Battery} * V_{of \text{ sys nominal}} * I_{max-PV}} \\
 &= \frac{9180 \text{ W}}{7 * 0.90 * 0.85 * 0.8 * 12 * 8.957} \\
 &= 19.93 \text{ modules} \\
 &\approx 20 \text{ modules}
 \end{aligned}$$

Series modules,

$$\begin{aligned}
 &= \frac{\text{System nominal voltage}}{\text{Nominal voltage of solar module}} \\
 &= \frac{12 \text{ V}}{12 \text{ V}} \\
 &= 1 \text{ modules}
 \end{aligned}$$

$$\begin{aligned}
 \text{Total modules} &= 20 * 1 \\
 &= 20 \text{ modules}
 \end{aligned}$$

Battery Sizing

$$\begin{aligned}
 \text{Parallel Batteries} &= \frac{\text{Total Energy in WH} * \text{Number of Days}}{n_{Inv} * n_{Battery} * V_{of \text{ sys nominal}} * \text{usage of battery}} \\
 &= \frac{9180 \text{ W} * 1 \text{ day}}{0.85 * 0.80 * 12 * 0.80} \\
 &= 1406.10 \text{ Ah}
 \end{aligned}$$

Battery capacity = 80%

I choose U-power 100A-12V GEL Battery,

Nominal voltage = 12 V
 Current I = 100 Ah

Parallel Battery = $1406.10 \text{ Ah} / 100\text{Ah}$
 = 14.061 batteries
 = 15 batteries

Series battery = Nominal voltage / Nominal V of battery
 = $12\text{V}/12\text{V}$
 = 1 battery

Total batteries = 15×1
 = 15 batteries

Sizing of Solar Charge Controller & PV Inverter

Sizing of Solar Charge Controller (A)


$$\begin{aligned} &= 20 \text{ parallel modules} * 8.95 * 1.25 & [\text{Isc} = 8.95 \text{ A}, \text{S.F.} = 1.25] \\ &= 223.75 \text{ A} \end{aligned}$$

Sizing of PV Inverter

$$\begin{aligned} &= \text{Total 5% power of entire building} * \text{S.F.} \\ &= 1.314 \text{ KW} * 1.25 \\ &= 1.6425 \text{ KW} \end{aligned}$$

S.F =1.25
Total 5% power of entire building = 1.314 KW]

Rooftop Solar PV Design & Setup

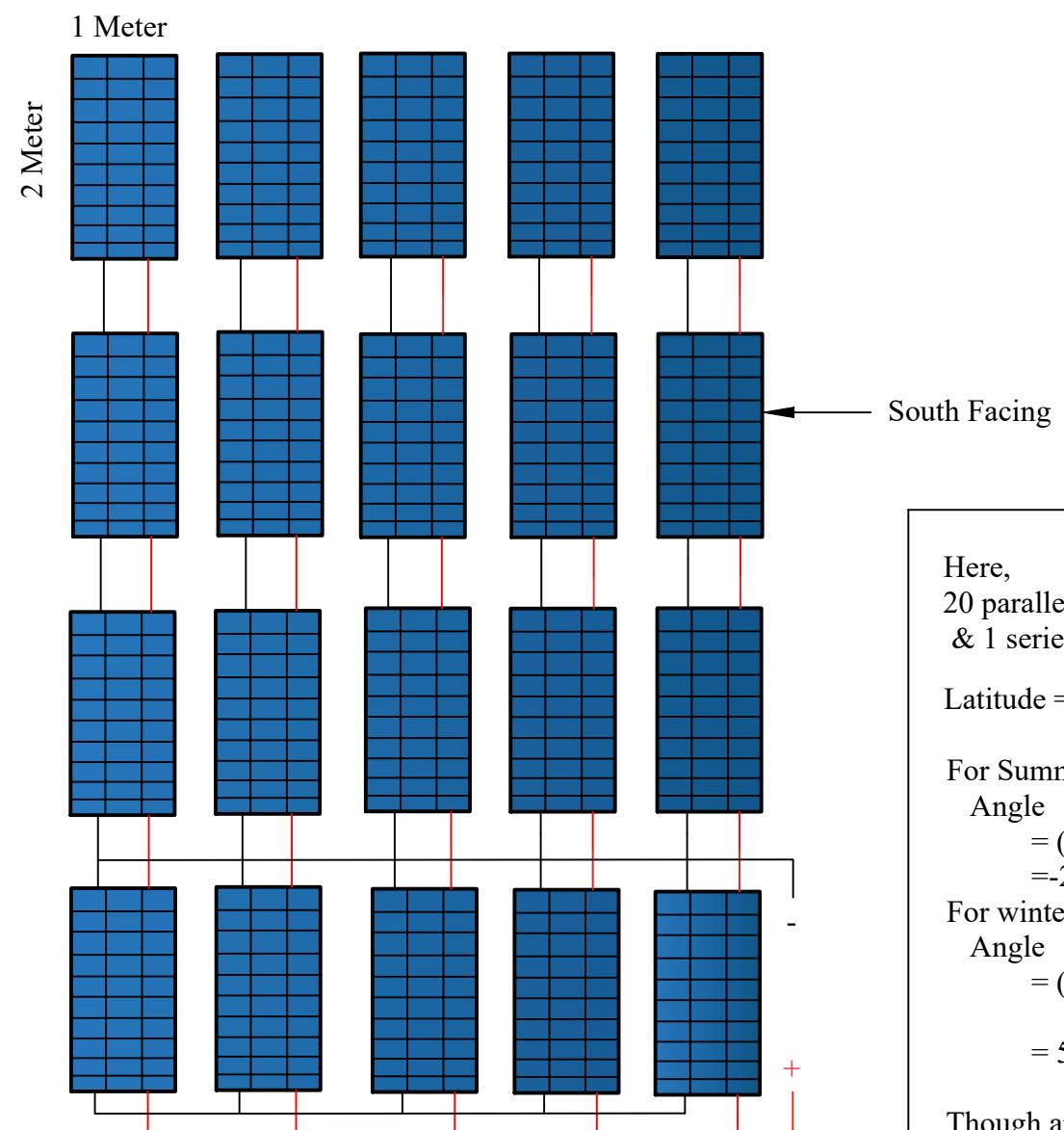


Here,
20 parallel modules
& 1 series modules

Latitude = 23.8 degree


For Summer,
Angle
 $= (23.8 * 0.9) - 23.5$
 $= -2.08$ degree

For winter,
Angle
 $= (23.8 * 0.9) + 29$
 $= 50.42$ degree

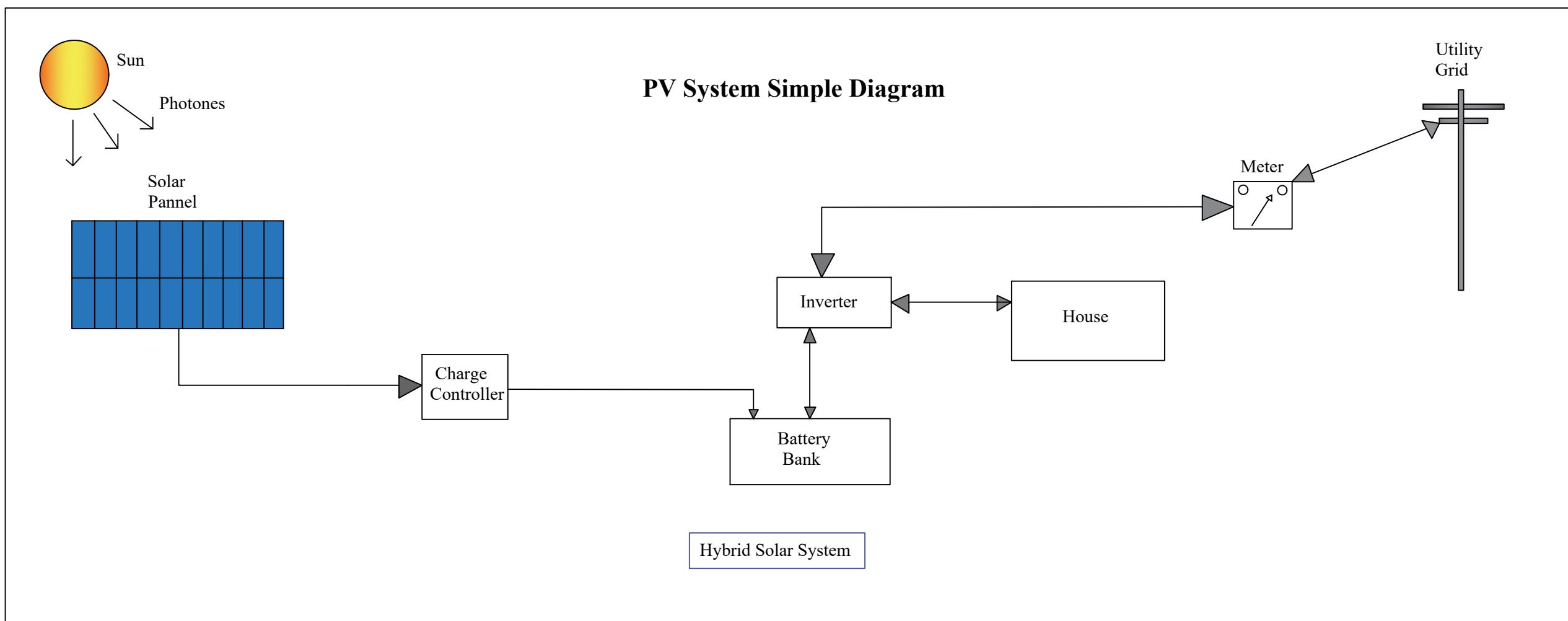Though angle is negative thus tilt
angle is 0 degree



Fire Safety System

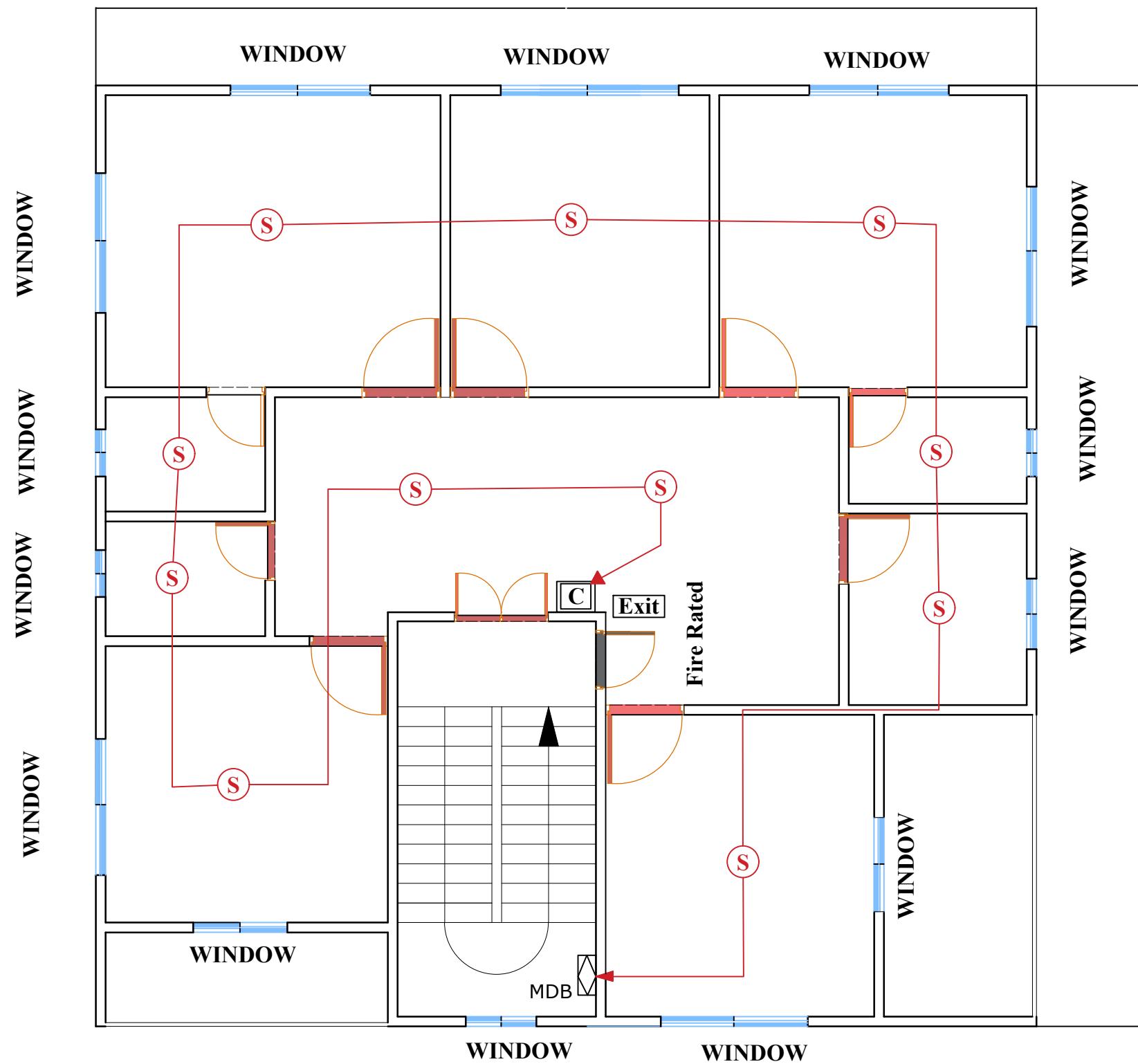

Symbol	Name
	MDB
	Control Panel
	Sensor

Wire colour
— red —

The End

Thank You